

Advanced Level Experimental Physics

86-Q₃: Resistivity, Using a Wheatstone Bridge


Time $1\frac{1}{2}$ hr.

Apparatus

Metre bridge & jockey; resistance wire (length $\approx 1\text{m}$, resistance $\approx 2\Omega$ but not less); metre rule; resistors (0.5Ω , 1Ω , $2 \times 2\Omega$, 5Ω , 10Ω , 20Ω); 1.5V cell; galvanometer; 4 connecting leads (3 long, 1 short); 1 sheet graph paper; micrometer.

The aim of this experiment is to determine the electrical resistivity of the wire provided. Proceed as follows:

- Set up a slide-wire metre bridge as illustrated below where E is a cell, G is a Galvanometer, length l of the resistance wire is connected across the right-hand gap of the bridge, and the jockey or slider J is placed at the 50cm mark.
- With $R = 20\Omega$, find the value of length l for which the galvanometer gives zero deflection when the slider is tapped onto the 50cm mark as shown below. (2 Marks)
- Repeat the procedure in (b) for values of R equal to 10Ω , 5Ω , 2Ω , 1Ω , and 0.5Ω . (8 marks)

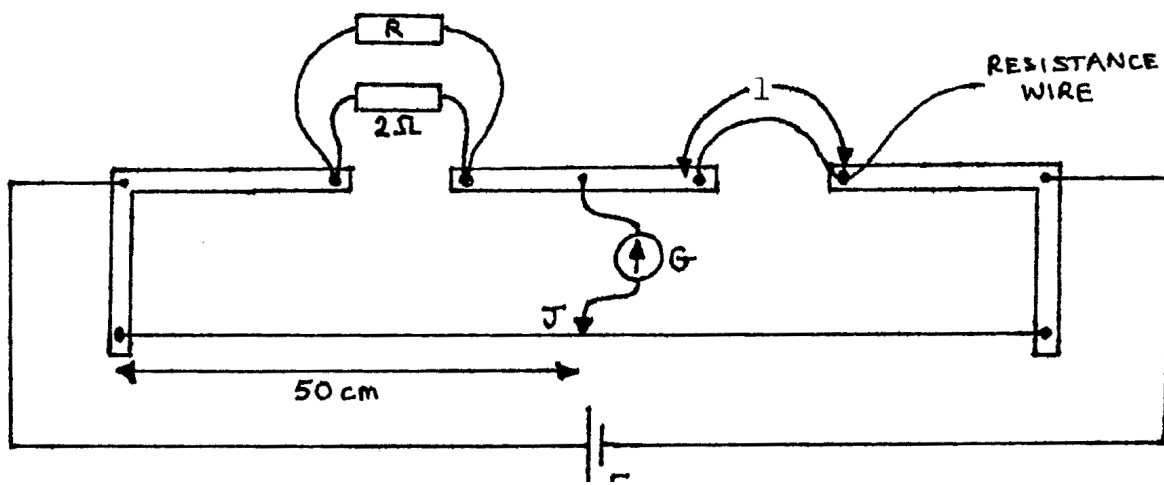

- i. Calculate and tabulate the values of $\frac{1}{R}$ and $\frac{1}{l}$ for the values of R equal to 20Ω , 10Ω , 5Ω , 2Ω , 1Ω , and 0.5Ω obtained in (b) and (c) above. (7 marks)
- ii. By means of the micrometer screw gauge provided, measure the diameter of the resistance wire, and hence calculate its average diameter d . (5 marks)
- iii. Plot a graph of $\frac{1}{R}$ vs. $\frac{1}{l}$ (whose values are recorded in i above) and determine the gradient. (12, 5 marks)
- iv. Determine the resistivity ρ of the resistance wire given that:

$$\frac{1}{R} = \frac{A}{\rho} \frac{1}{l} - \frac{1}{2}$$

Where A is the cross-sectional area of the resistance wire. (4, 7 marks)

© 2015 [CC-BY](#) by Bob Drach and Norman Price
Based off of book published ???
[About](#)