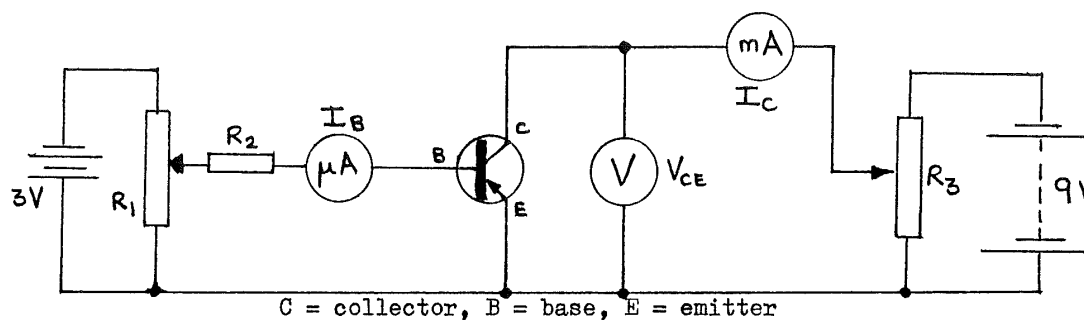


G2-1: Transistor Characteristics

Apparatus

3V battery; 9V battery; 2 rheostats (high resistance); resistor R_2 (approx. $50\text{ k}\Omega$); voltmeter (0–5 Vdc); ammeter ($\approx 50\mu\text{A fsd}$); ammeter ($\approx 3\text{ mA fsd}$); transistor (pnp); connecting leads (12 short); 2 sheets graph paper.



Instructions

Set up the circuit as above, but do not connect the batteries until a teacher has checked the circuit (to avoid damaging the ammeters or transistor). In the experiment, when not taking readings, leave the batteries disconnected.

EXPERIMENT I

To investigate the 'transfer characteristics' of the transistor. The transistor acts as a current amplifier: the size of the large current I_C depends on the size of the small current I_B . The circuit used above is called a 'common emitter' circuit.

I: Procedure

1. Set V_{CE} to 4V using rheostat R_3 . Ensure that this remains constant (adjust R_3 again later as necessary).
2. Set I_B to 0 using R_1 . Read and note I_B and I_C .
3. Increase I_B a little using R_1 , and read and note I_B and I_C . Continue increasing I_B and reading the ammeters until $I_C = 3$ mA.
4. Tabulate the readings of I_E , I_C , and the value of V_{CE} .

1: Analysis

1. Plot a graph of I_C against I_B , labelling the curve with the value of V_{CE} used.
2. Find the gradient of the straight-line section of the curve. Then:

$$\text{Current gain } \beta = \frac{\Delta I_C}{\Delta I_B} = \text{gradient}$$

EXPERIMENT 2

To study how I_C varies when V_{CE} is changed, for certain fixed values of I_B . The graph obtained is called the 'output characteristic' of the transistor.

2: Procedure


1. Set $I_B = 0$ using R_1 . Starting with $V_{CE} = 0$, and little by little increasing V_{CE} up to 5V, take a set of readings of I_C and V_{CE} and note the value of $I_B = 0$.
2. Increase I_B to $10\mu\text{A}$, and obtain another set of readings of I_C and V_{CE} as in step 1.
3. Repeat the procedure with $I_B = 20\mu\text{A}$ then $30\mu\text{A}$.
4. Tabulate the sets of readings of I_C and V_{CE} , noting the value of I_B for each set.

2: Analysis

1. Plot a graph of I_C vs. V_{CE} to obtain four curves. Label each curve with the appropriate value of I_B used.

Questions

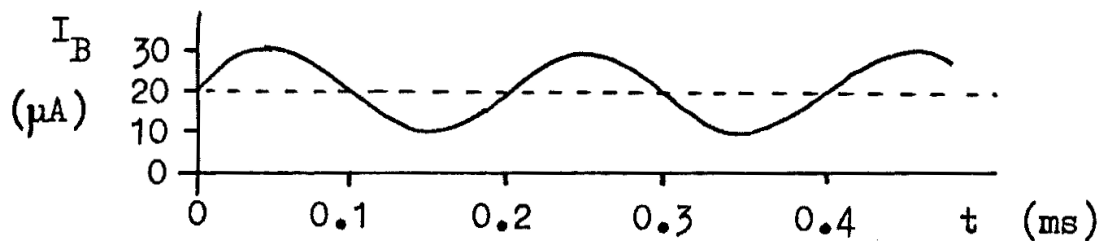1. When $I_B = 0$, I_C should be zero for all V_{CE} . However all transistors have some 'leakage current.' What is the value of the leakage current I_C when $V_{CE} = 4V$?
2. What is the approximate minimum V_{CE} so that a variation in I_B between 0 and $30\mu A$ produces a large change in I_C ? (In practice the supply voltage is usually set between this value and a certain maximum. The maximum depends on the 'breakdown voltage' of the junctions).
3. In use as an amplifier, an AC input voltage makes I_B vary with time. For example:



- a. Use the value of β to make a graph of I_C against time.
 - b. If a resistor $R = 1k\Omega$ is connected in series with the collector C , so that I_C flows through it; draw a graph of the potential difference (p.d.) across this resistor against time.
 - c. What is the frequency of these AC currents and p.d.?
4. Draw a diagram to show while the pnp transistor is conducting:
 - a. Electron flows and conventional currents through the three terminals.
 - b. Electron & hole movements inside the transistor (may be simplified).

