

F6-1: Self Inductance in AC Circuits


Apparatus

300 turn coil; 2 iron C-cores; C-core clip; ammeter (0 – 1 Adc); voltmeter (0 – 5 Vdc); 3 batteries (3V); 2 x 100Ω resistors; CRO (oscilloscope); AC power supply; 0.5m ruler; connecting leads (5 short); 1 sheet graph paper.


NB: This experiment requires mains electricity.

Procedure

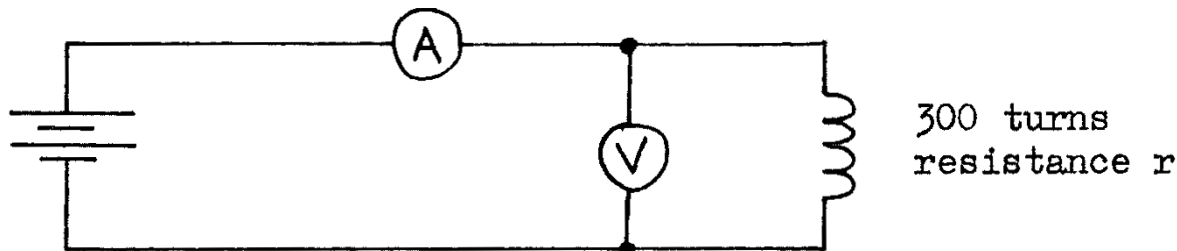1. To find the resistance r of the coil, connect the following circuit and use the readings of the ammeter and voltmeter to calculate r :




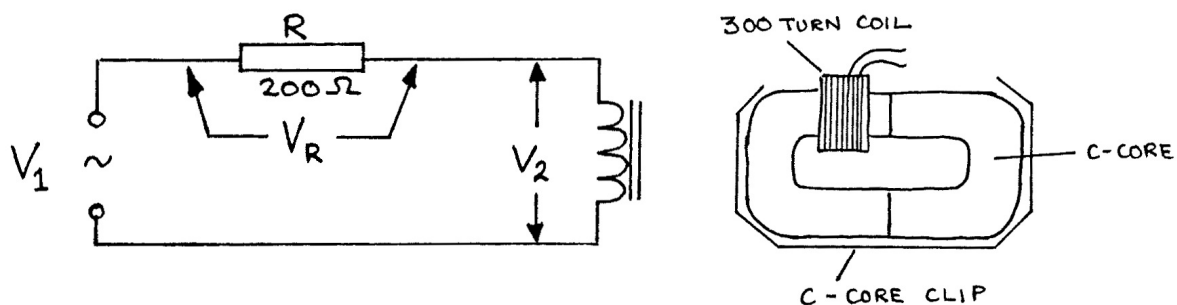2. To find the inductance L of the coil with an iron core, connect the following circuit:



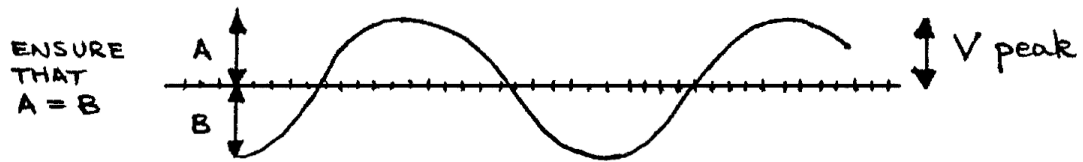
- a. Connect the CRO input to V_1 . Adjust the CRO so that V_1 is about 4V, the supply

being switched to AC. Adjust the CRO so that the AC waveform is seen clearly:




Carefully adjust the power supply so that the peak value of V_1 as seen on the screen is 4V peak.

- Now connect the CRO to measure V_R peak. Use this, and the value of R to calculate the value of I peak for the circuit.
- Use the CRO to measure V_2 peak.
- Repeat a), b), and c), but using V_1 of 3.5, 3, 2.5, 2, 1.5, 1, 0.5, and 0 volt peak each time.
- Tabulate the values of V_R peak, V_2 peak, and I peak.
- Measure the cross-sectional area of the iron core and the distance l around the centre of the pair of cores as shown below:

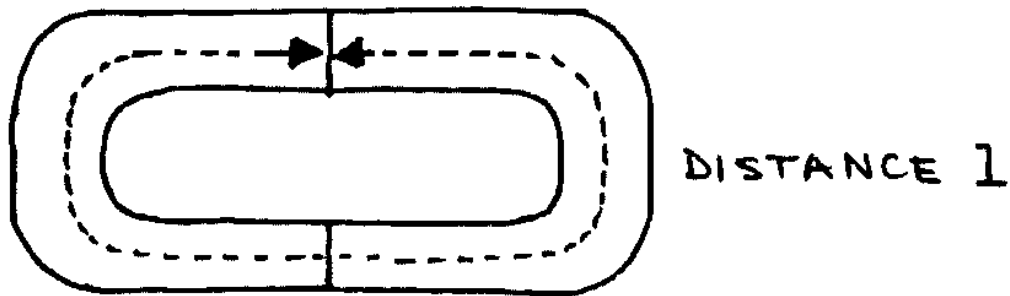

Theory

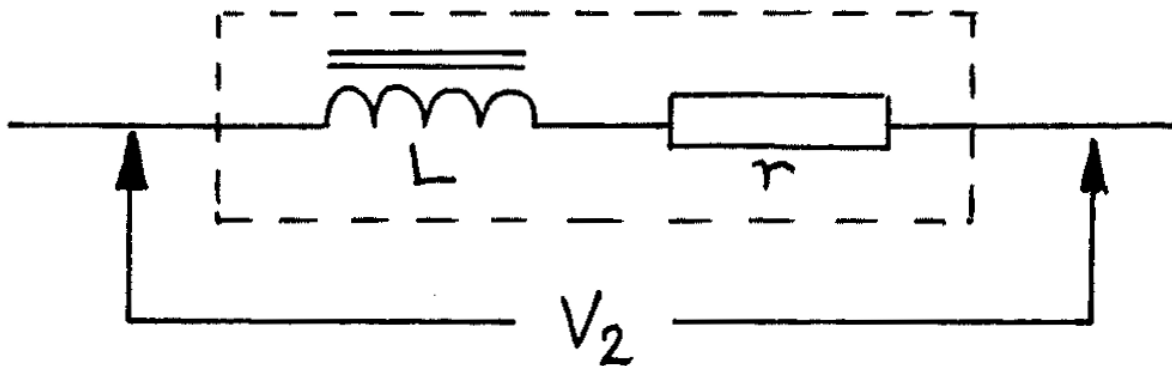The coil with its iron core has an inductance L , and the copper wire of the coil has a resistance r . An equivalent circuit for the coil is:



The impedance of this combination of r and L is given by:

$$Z = \sqrt{r^2 + \omega^2 L^2} \quad \text{--- equation 1}$$

$$\begin{aligned} \text{where: } Z &= \frac{V_2 \text{ rms}}{I \text{ rms}} = \frac{V_2 \text{ peak}}{I \text{ peak}} & \text{--- equation 2} \\ \text{and: } \omega &= 2\pi f \end{aligned}$$

It is also possible to calculate L using data about the coil and its core:

$$L = \frac{\mu_0 \mu_r N^2 A}{l} \quad \text{--- equation 3}$$

where: $\mu_0 = 4\pi \times 10^{-7} \text{ Hm}^{-1}$
 μ_r = relative permeability of the iron
 N = number of coil turns
 A = core cross-sectional area
 l = distance around core

Analysis

1. Plot a graph of V_2 peak against I peak, and find the gradient.
2. Use the gradient and equation 2 to find the value of Z .
3. Use equation 1 to find the inductance of the coil, L .
4. Use this value of L , together with the other measured values, and equation 3, to find the relative permeability of this type of iron, μ_r .

5. Look up values of μ_r for different types of iron in a reference table and try to deduce the type of iron alloy used in your iron cores.

Questions

1. Use the values of R , r , and L above to calculate the current I_{peak} when $V_1 = 8\text{V}$ peak and $f = 1\text{kHz}$.
2. Use equation 3 to estimate L if the iron core is removed. Show that in this case $Z \approx r$. Repeat Q1 using L for the coil without an iron core.
3. Briefly explain the energy changes in r and L when:
 - a. The current is + and rising
 - b. The current is a maximum +, and constant
 - c. the current is + and falling
4. How can an inductor be constructed so that power losses are kept to a minimum (consider both the design of the coil and the core)?
5. Why is it desirable to keep power losses to a minimum in an inductor used in the tuning circuit of a radio receiver?
6. Prove that:

$$\frac{V_2 \text{ rms}}{I \text{ rms}} = \frac{V_2 \text{ peak}}{I \text{ peak}} \quad (\text{from equation 2})$$

Why in the experiment is V_{peak} measured rather than V_{rms} ?

7. Sketch on the same graph curves of V and I for an inductor (with $r = 0$) which is connected to an AC power supply.
8. Explain carefully why $V_1 \text{ peak} \neq V_R \text{ peak} + V_2 \text{ peak}$.